

Truth Tables | Part B

OR is a logic gate which outputs 1 if either or both of the inputs are 1. Otherwise it outputs 0. Here is what the truth table looks like. Again, as you can see, there are four different combinations of input value. The OR gate only needs 1 of the inputs to be 1 for the output to be 1.