

Truth Tables | Part C

NOT is a logic gate which outputs the opposite value to what was input. Here is what the truth table looks like. As you can see, there are only two different combinations of input value. The NOT gate gives the opposite to what was input. So if the input is 0, it produces a 1 and vice versa.