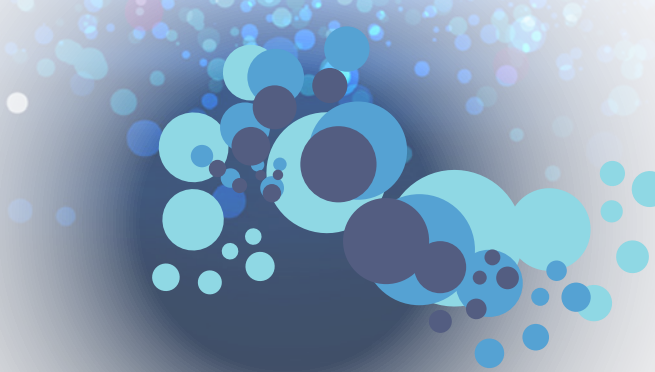




# Truth tables


## Teacher's Notes

## Lesson Plan

Length	60 mins	Specification Link	2.1.2/f	Binary logic
Learning objective	Students should be able to (a) produce a truth table from a given logic diagram			
Time (min)	Activity	Further Notes		
10	<p>Using a projector show the <b>Starter Activity</b>.</p> <p>Ask the students to predict what should be selected for each of the logical arguments and then display the results.</p> <p>The reset button will then display all of the elements.</p> <p>Inform the students that they have been investigating Boolean logic, first proposed by George Boole in the 1800s.</p> <p>In Boolean algebra, all values can be reduced to 'true' or 'false' and is therefore important in the operation of computers as it coincides with the binary numbering system.</p> <p>Show students the link to the specification. Explain the purpose and objectives of the lesson.</p>	NB press the reset button between buttons, otherwise only the results currently displayed will appear.		
5	Watch the set of videos.			
5	<p>Ask some questions about the videos to assess learning. For example:</p> <ul style="list-style-type: none"> <li>• What is a truth table?</li> <li>• What are the shapes of the symbols used to represent AND, OR and NOT?</li> </ul>	A table that displays all the possible results of a logic function.		
20	<p><b>Worksheet 1</b></p> <p>Students to complete Worksheet 1 either on paper or on a computer.</p> <p>Ask individual students for their answers and discuss with the class so that all students will have the correct answers entered on their worksheets.</p>	Answers provided.		

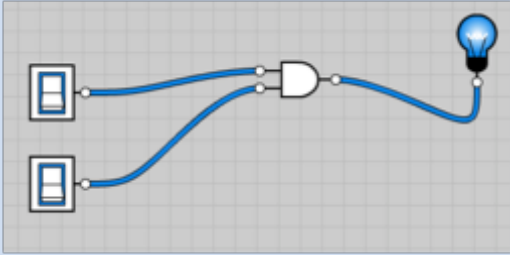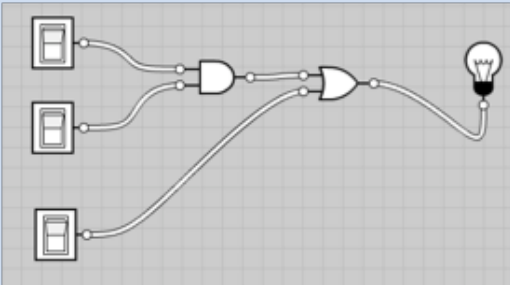

Time (min)	Activity	Further Notes																																								
15	<p>The students should now use the Kent State University logic gate simulator. (<a href="http://www.cambridgegcseccomputing.org/weblink9">http://www.cambridgegcseccomputing.org/weblink9</a>)</p> <p>The students can simulate the operation of logic gates and switches.</p>  <p>They should demonstrate all of the examples in Worksheet 1 and compound operations e.g. AND with NOT</p>	<p>Instructions for using this resource may be found in the help section at the top of the webpage.</p>																																								
	<p><b>Extension Challenge/Homework</b></p> <p>The students should complete and submit Worksheet 2.</p>																																									
5	<p><b>Plenary</b></p> <p>Display the following example:</p>  <p>Ask the students to produce a truth table for this function.</p>	<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>C</th> <th>Q</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	A	B	C	Q	0	0	0	0	1	0	0	0	1	1	0	1	0	1	0	0	0	1	1	1	0	0	1	1	1	0	1	1	0	1	1	1	1	1	1	1
A	B	C	Q																																							
0	0	0	0																																							
1	0	0	0																																							
1	1	0	1																																							
0	1	0	0																																							
0	1	1	1																																							
0	0	1	1																																							
1	0	1	1																																							
0	1	1	1																																							
1	1	1	1																																							

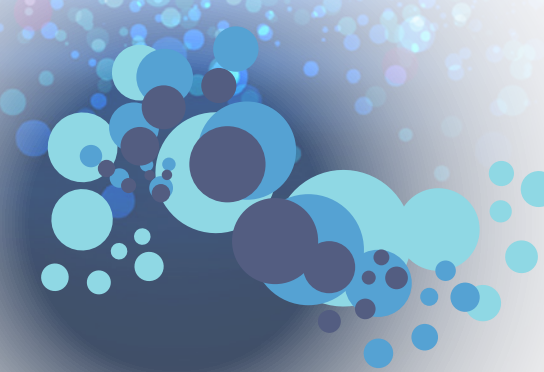

## WORKSHEET 1 ANSWERS

**1** (a) Explain what is meant by the following terms:

(i) Binary digit

Either of the digits 0 or 1 used in the binary number system. It is shortened to the term 'bit'.

(ii) Byte

A unit that usually consist of 8 bits. A byte is the number of bits needed to encode a single character of text and is the smallest addressable unit of memory.

(b) Explain what is meant by a 'nibble' and why it is used in computing.

A nibble consists of 4 bits or half a byte. As there are possible values, so a nibble corresponds to a single hexadecimal digit. Therefore an eight digit byte can be represented by two digits of hexadecimal.

**2** Split the following bytes into nibbles and then convert them to hex. Write your answers in the spaces provided.

(a) **1 1 0 1 0 0 1 1**

Nibbles

Hex

(b) **0 1 1 0 0 1 1 0**

Nibbles

Hex

(c) **1 1 1 1 0 0 1 1**

Nibbles

Hex

**3** In the spaces below place the following into ascending order according to size.

Megabyte Bit Nibble Terabyte Byte Gigabyte Kilobyte


## WORKSHEET 2 ANSWERS

1 Complete the following sentence:


Logic gates are switches which perform a logical function on one or more logical inputs and produce a single logical **output**.

2 In the spaces below draw the symbols used to represent the following logic gates.


AND

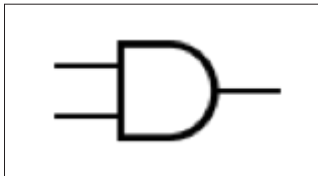

OR

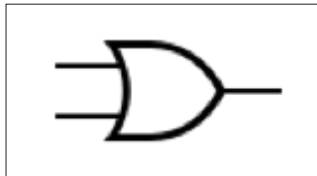

NOT

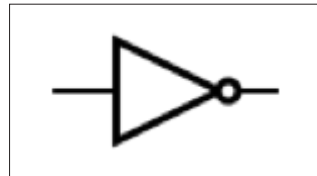

3 Complete the following sentence:

A truth table is a breakdown of a logic function by listing all possible **values** the function can attain.


4 Complete the truth tables for the following gates.

(a)


Symbol	Truth table		
	A	B	Q
	0	0	0
	0	1	1
	1	0	1
	1	1	1
	1	1	1

## WORKSHEET 1 ANSWERS


- 4 Complete the truth tables for the following gates.  
(b)

Symbol	Truth table		
	<b>A</b>	<b>B</b>	<b>Q</b>
	0	0	0
	0	1	0
	1	0	0
	1	1	1

(c)

Symbol	Truth table	
	<b>A</b>	<b>B</b>
	0	1
	1	0

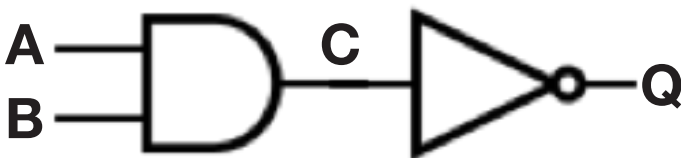- 5 (a) Complete the truth table for the following combination.



A	B	C	D
0	0	0	1
1	0	0	1
0	1	0	1
1	1	1	0

- (a) Give the logic statement for this combination.


$$Q = \text{NOT} (A \text{ AND } B)$$

## WORKSHEET 1 ANSWERS

6

Give the logic gate drawing and the truth table for the following logic statement.

$$Q = \text{NOT } (A \text{ OR } B)$$

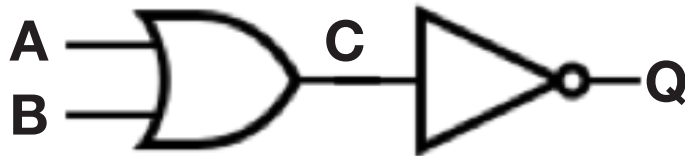

A	B	C	D
0	0	0	1
1	0	1	0
0	1	1	0
1	1	1	0

## WORKSHEET 2 ANSWERS

1

A	B	P
0	0	0
0	1	1
1	0	0
1	1	0

2

1,1 1 1