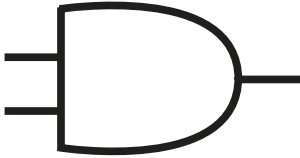
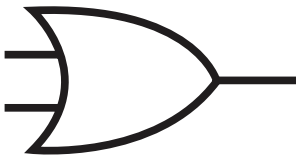
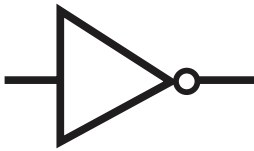


# Logic gates AND, OR, NOT

## Worksheet 1

 <p>AND</p>	An AND gate will combine the Boolean values of two inputs. If both inputs are true the output will be true. If any of the inputs are false it will output false.
 <p>OR</p>	An OR gate will combine the Boolean values of two inputs. If one or more inputs are true then the output will be true.
 <p>NOT</p>	A NOT gate will always give an output that is opposite to what the input is.

1 What does the term Boolean mean?

---

---

2 Create *four* different diagrams with *two* or *three* logic gate symbols in each one.