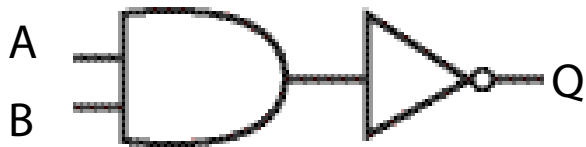


Logic gates AND, OR, NOT

Worksheet 2

- 1 Write a Boolean logic expression for the output Q of this logic circuit in terms of the inputs A and B:



Q =

- 2 Draw the logic circuit for the following expression:

$$Q = (A \text{ OR } B) \text{ AND } C$$